



Orange
Digital Center

Orange Digital Center

Digital Design and FPGA Flow

Assignment 3

Week 3

Created By: Ahmed Mostafa Gomaa

Submitted to :

Dr. Tamer Saleh

Eng. Asmaa El-sayed

Eng. Nourhan

Table of Contents

1. Introduction.....	3
2. Sequence Detector	4
2.1. Introduction.....	4
2.2. Overlapping Sequence Detector For (1010110).....	4
2.3. Moore	4
2.4. FSM Diagram.....	5
2.5. Code Verilog.....	5
2.6. RTL Viewer	6
2.7. Timing Diagram	6
2.8. Mealy	6
2.9. FSM Diagram.....	6
2.10. Code Verilog.....	7
2.11. RTL Viewer	7
2.12. Timing Diagram	7
3. Testbench.....	8
3.1. Introduction.....	8
3.2. Testbench for Carry Lock ahead	8
3.3. Timing Diagram	8

1. Introduction

Finite State Machines (FSMs)

A **Finite State Machine (FSM)** is a computational model used to design sequential logic circuits and systems. It consists of a finite number of states, transitions between those states, and actions associated with transitions or states. FSMs are widely used in digital design to model systems that respond to inputs over time, such as control units, communication protocols, and user interfaces.

An FSM is defined by:

1. **States:** The system's possible conditions or modes.
2. **Transitions:** Rules that dictate how the system moves from one state to another based on inputs.
3. **Actions:** Operations performed during transitions or while in a specific state.

FSMs can be classified into two types:

- **Moore Machine:** Outputs depend only on the current state.
- **Mealy Machine:** Outputs depend on both the current state and inputs.

Testbenches

A **testbench** is a virtual environment used to verify the functionality of a digital design, such as an FSM, through simulation. It provides input stimuli to the design and monitors its outputs to ensure it behaves as expected. Testbenches are essential for debugging and validating designs before they are implemented in hardware.

Key components of a testbench include:

1. **Input Stimuli:** Simulated inputs to drive the design.
2. **Design Under Test (DUT):** The FSM or circuit being tested.
3. **Output Monitoring:** Observing and comparing outputs against expected results.
4. **Clock and Reset Signals:** Essential for synchronizing and initializing the design.

Why Combine FSMs and Testbenches?

FSMs are often used in complex systems where correct behavior is critical. A testbench allows designers to:

- Verify state transitions and outputs under various conditions.
- Detect and fix errors early in the design process.
- Ensure the FSM meets design specifications before implementation.

By simulating an FSM with a testbench, designers can confidently proceed to hardware implementation, knowing the design has been thoroughly tested. This combination is a cornerstone of reliable digital system design.

2. Sequence Detector

2.1. Introduction

A **sequence detector** is a fundamental component in digital systems used to identify a specific pattern of bits in a stream of input data. It plays a crucial role in communication systems, digital signal processing, and error detection mechanisms. Sequence detectors can be implemented using **finite state machines (FSMs)**, which transition between different states based on the incoming bit sequence.

There are two main types of sequence detectors:

1. **Overlapping Sequence Detector** – Detects a sequence even if part of it overlaps with the previous sequence.
2. **Non-Overlapping Sequence Detector** – Requires the sequence to restart after a successful detection.

These detectors are commonly built using flip-flops and logic gates in hardware or programmed using Verilog or VHDL in FPGA-based designs. Their applications include **data synchronization, protocol validation, and security systems** where specific bit patterns need to be identified efficiently.

2.2. Overlapping Sequence Detector For (1010110)

2.3. Moore

A **sequence detector** identifies a specific pattern in a stream of input bits. In this case, we are designing a **Moore finite state machine (FSM)** to detect the "1010110" sequence with overlapping allowed.


Moore Machine Overview

A **Moore FSM** determines its output based **only on the current state**, unlike a **Mealy FSM**, which depends on both the state and input. This means the output changes **only when transitioning to a new state** and is not directly affected by the current input.

State Diagram and Explanation

To detect the pattern **1010110** in an **overlapping manner**, we need to track partial matches and move through states accordingly. Each state represents the progress in matching the sequence.

2.4. FSM Diagram

 

2.5. Code Verilog

```

module DETECTOR MOORE (
    input wire clk ,
    input wire reset ,
    input wire in ,
    output reg detected
);

parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011,
           S4 = 3'b100, S5 = 3'b101, S6 = 3'b110, S7 = 3'b111;

reg [2:0] current_state, next_state;


always @(posedge clk or posedge reset) begin
    if (reset)
        current_state <= S0;
    else
        current_state <= next_state;
end

always @(*) begin
    case (current_state)
        S0: next_state = (in) ? S1 : S0;
        S1: next_state = (in) ? S1 : S2;
        S2: next_state = (in) ? S3 : S0;
        S3: next_state = (in) ? S1 : S4;
        S4: next_state = (in) ? S5 : S0;
        S5: next_state = (in) ? S6 : S4;
        S6: next_state = (in) ? S1 : S7;
        S7: next_state = (in) ? S3 : S0;
        default: next_state = S0;
    endcase
end


// Output Logic (Moore FSM: Output depends only on the state)
always @(posedge clk or posedge reset) begin
    if (reset)
        detected <= 0;
    else
        detected <= (current_state == S7); // Output high when full sequence detected
    end
endmodule

```

2.6. RTL Viewer

 

2.7. Timing Diagram

 


2.8. Mealy

An **overlapping sequence detector** is a digital system designed to identify a specific sequence of bits in a continuous stream of input data. Unlike non-overlapping detectors, an overlapping detector allows the detected sequence to share bits with subsequent sequences, making it more efficient for continuous data processing.

In this context, we focus on designing a **Mealy Machine** to detect the sequence "1010110". A Mealy Machine is a type of Finite State Machine (FSM) where the outputs depend on both the current state and the inputs. This makes it particularly suitable for sequence detection, as the output can immediately reflect whether the desired sequence has been detected.

2.9. FSM Diagram

 

2.10. Code Verilog

```

module DETECTOR_MEALY (
    input wire clk ,
    input wire reset ,
    input wire in ,
    output reg detected
);

    parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011,
               S4 = 3'b100, S5 = 3'b101, S6 = 3'b110;

    reg [2:0] current_state, next_state;

    always @(posedge clk or negedge reset) begin
        if (!reset)
            current_state <= S0;
        else
            current_state <= next_state;
    end


    always @(*) begin
        case (current_state)
            S0: next_state = (in) ? S1 : S0;
            S1: next_state = (in) ? S1 : S2;
            S2: next_state = (in) ? S3 : S0;
            S3: next_state = (in) ? S1 : S4;
            S4: next_state = (in) ? S5 : S0;
            S5: next_state = (in) ? S6 : S4;
            S6: next_state = (in) ? S1 : S2;
            default: next_state = S0;
        endcase
    end

    always @(*) begin
        detected <= (current_state == S6) & ( in == 0 ) ;
    end


endmodule

```

2.11. RTL Viewer

 

2.12. Timing Diagram

 

3. Testbench

3.1. Introduction

A **testbench** is a critical tool in digital design and verification, used to simulate and validate the functionality of a hardware design before it is implemented in physical hardware. It acts as a virtual environment where designers can apply input stimuli to a **Design Under Test (DUT)** and observe its outputs to ensure it behaves as expected. Testbenches are essential for debugging, verifying correctness, and ensuring that the design meets its specifications.

3.2. Testbench for Carry Look ahead

```
`timescale 1ns/1ps
module CARRY_LOCK_AHEAD_TB;

    reg [3:0] A, B;
    reg      C_IN;
    wire [3:0] S;
    wire      C_OUT;

    CARRY_LOCK_AHEAD DUT (
        .A(A),
        .B(B),
        .C_IN(C_IN),
        .S(S),
        .C_OUT(C_OUT)
    );

    initial begin
        A = 4'b0000; B = 4'b0000; C_IN = 0; #10;
        A = 4'b0001; B = 4'b0001; C_IN = 0; #10;
        A = 4'b0011; B = 4'b0011; C_IN = 0; #10;
        A = 4'b0101; B = 4'b0011; C_IN = 1; #10;
        A = 4'b1111; B = 4'b0001; C_IN = 0; #10;
        A = 4'b1010; B = 4'b0101; C_IN = 1; #10;
        A = 4'b1111; B = 4'b1111; C_IN = 1; #10;
    end
endmodule
```

3.3. Timing Diagram

